

## Q1. 2 BIT COMPARATOR USING TERNARY OPERATOR.


### VERILOG CODE:

```
module comparator2bit(A,B,E,G,L);  
    input [1:0]A,B;           // Declare 2-bit input ports A and B  
    output E,G,L;             // Declare output ports: E for Equal, G for Greater, L for Less  
    assign E=(A==B)?1'b1:1'b0; // If A is equal to B, set E to 1 (true), else 0 (false)  
    assign G=(A>B)?1'b1:1'b0;  // If A is greater than B, set G to 1 (true), else 0 (false)  
    assign L=(A<B)?1'b1:1'b0;  // If A is less than B, set L to 1 (true), else 0 (false)  
endmodule
```

### TEST BECH CODE:

```
module comparator2bit_test;  
    reg [1:0]A,B;  
    wire E,G,L;  
    comparator2bit dut(A,B,E,G,L);  
    initial begin  
        A=2'b00; B=2'b00;  
        #5 A=2'b00; B=2'b01;  
        #5 A=2'b01; B=2'b00;  
        #5 A=2'b01; B=2'b01;  
    end  
    initial begin  
        $monitor("Sim time=%0t,A=%b,B=%b,E=%b,G=%b,L=%b", $time,A,B,E,G,L);  
    end  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(0,A,B,E,G,L);  
    end  
endmodule
```

**OUTPUT WAVEFORM:**

 

**SIMULATION OUTPUT:**

Sim time=0,A=00,B=00,E=1,G=0,L=0  
Sim time=5,A=00,B=01,E=0,G=0,L=1  
Sim time=10,A=01,B=00,E=0,G=1,L=0  
Sim time=15,A=01,B=01,E=1,G=0,L=0