

# STRUCTURAL PROGRAMMING

## Q1.FULL ADDER USING HALF ADDER:

### VERILOG CODE:

//Lower level model

```
module HA(A,B,Sum,Cout);
```

```
    input A,B;                // Inputs: A and B
```

```
    output Sum,Cout;          // Outputs: Sum and Carry-out (Cout)
```

```
    assign Sum=A^B;           // Sum is the XOR of A and B
```

```
    assign Cout=A&B;          // Carry-out is the AND of A and B
```

```
endmodule
```

//Top level Model Full Adder

```
`include "HA.v"              // Include the Half Adder module
```

```
module FA(A,B,Cin,Sum,Cout);
```

```
    input A,B,Cin;            // Inputs: A, B, and Carry-in (Cin)
```

```
    output Sum,Cout;          // Outputs: Sum and Carry-out (Cout)
```

```
    wire w1,w2,w3;            // Internal wires to connect the half adders
```

```
    HA h1(A,B,w1,w2);          // First half adder: adds A and B
```

```
    HA h2(w1,Cin,Sum,w3);       // Second half adder: adds w1 and Cin to produce the final Sum
```

```
    assign Cout=w2|w3;         // Final Carry-out is the OR of two intermediate carries
```

```
endmodule
```

### TEST BENCH CODE:

```
module FA_test;
```

```
    reg A,B,Cin;
```

```
    wire Sum,Cout;
```

```
    FA dut(A,B,Cin,Sum,Cout);
```

```
    initial begin
```

```
        A=1'b0; B=1'b0; Cin=1'b0;
```

```
        #5 A=1'b0; B=1'b0; Cin=1'b1;
```

```
        #5 A=1'b0; B=1'b1; Cin=1'b0;
```

```

#5 A=1'b0; B=1'b1; Cin=1'b1;

#5 A=1'b1; B=1'b0; Cin=1'b0;

#5 A=1'b1; B=1'b0; Cin=1'b1;

#5 A=1'b1; B=1'b1; Cin=1'b0;

#5 A=1'b1; B=1'b1; Cin=1'b1;

end

initial begin

    $monitor("Sim
        time=%0t,A=%b,B=%b,Cin=%b,Sum=%b,Cout=%b",$time,A,B,Cin,Sum,Cout);

end

initial begin

    $dumpfile("dump.vcd");


    $dumpvars(0,A,B,Cin,Sum,Cout);

end

endmodule

```

## OUTPUT WAVEFORMS:

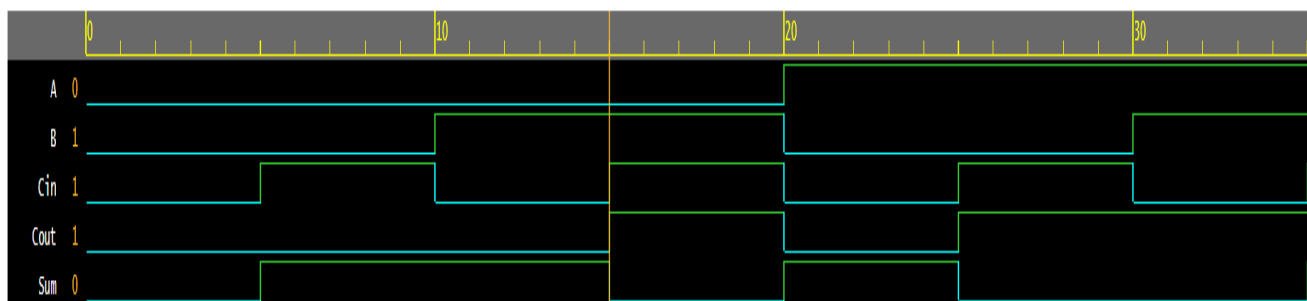

## SIMULATION OUTPUT:

```

Sim time=0,A=0,B=0,Cin=0,Sum=0,Cout=0
Sim time=5,A=0,B=0,Cin=1,Sum=1,Cout=0
Sim time=10,A=0,B=1,Cin=0,Sum=1,Cout=0
Sim time=15,A=0,B=1,Cin=1,Sum=0,Cout=1
Sim time=20,A=1,B=0,Cin=0,Sum=1,Cout=0
Sim time=25,A=1,B=0,Cin=1,Sum=0,Cout=1
Sim time=30,A=1,B=1,Cin=0,Sum=0,Cout=1
Sim time=35,A=1,B=1,Cin=1,Sum=1,Cout=1

```